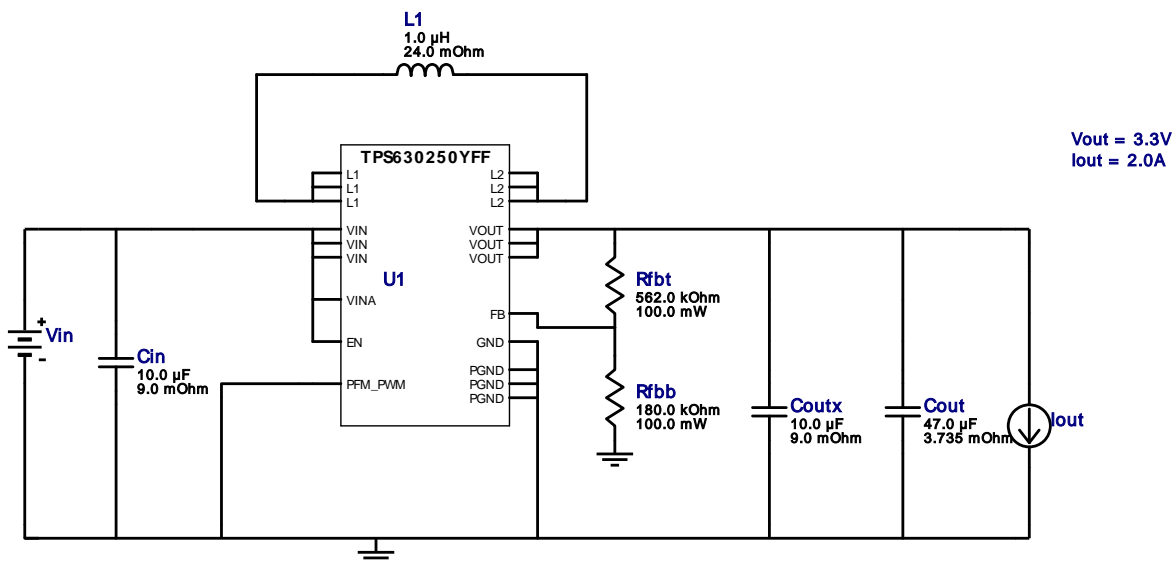








## WEBENCH® Design Report







Design : 5175827/7 TPS630250YFFR  
TPS630250YFFR 2.7V-4.1V to 3.30V @ 2.0A




### Electrical BOM

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	Cin	MuRata	GRM188R60J106ME47D Series= X5R	Cap= 10.0 uF ESR= 9.0 mOhm VDC= 6.3 V IRMS= 2.74 A	1	\$0.02	0603 5 mm <sup>2</sup>
2.	Cout	MuRata	GRM31CR60J476ME19L Series= X5R	Cap= 47.0 uF ESR= 3.735 mOhm VDC= 6.3 V IRMS= 4.091 A	1	\$0.11	1206_190 11 mm <sup>2</sup>
3.	Coutx	MuRata	GRM188R60J106ME47D Series= X5R	Cap= 10.0 uF ESR= 9.0 mOhm VDC= 6.3 V IRMS= 2.74 A	1	\$0.02	0603 5 mm <sup>2</sup>
4.	L1	Vishay-Dale	IHLP1212BZER1R0M11	L= 1.0 uH DCR= 24.0 mOhm	1	\$0.56	IHLP-1212BZ 19 mm <sup>2</sup>
5.	Rfbb	Yageo America	RC0603FR-07180KL Series= ?	Res= 180.0 kOhm Power= 100.0 mW Tolerance= 1.0%	1	\$0.01	0603 5 mm <sup>2</sup>
6.	Rfbt	Yageo America	RC0603FR-07562KL Series= ?	Res= 562.0 kOhm Power= 100.0 mW Tolerance= 1.0%	1	\$0.01	0603 5 mm <sup>2</sup>
7.	U1	Texas Instruments	TPS630250YFFR	Switcher	1	\$1.05	YFF0020AJAF 9 mm <sup>2</sup>

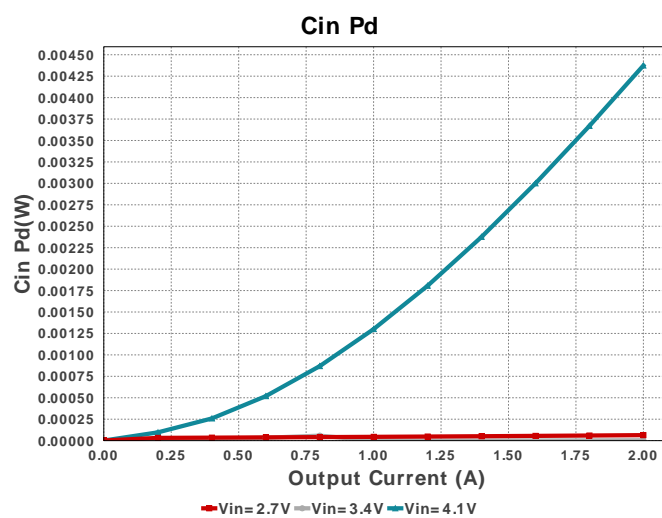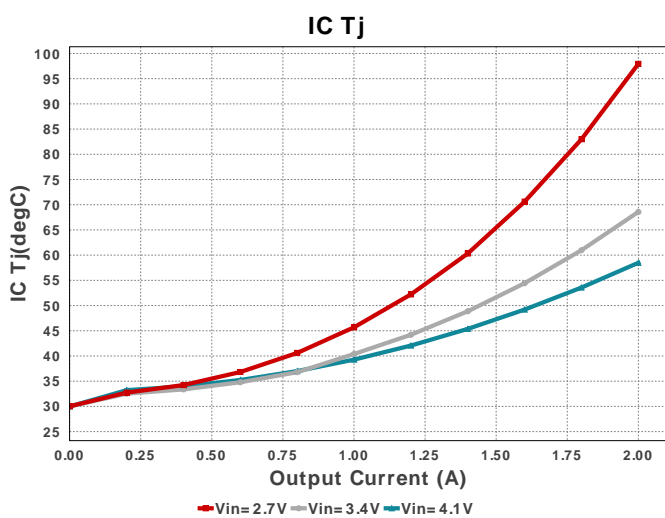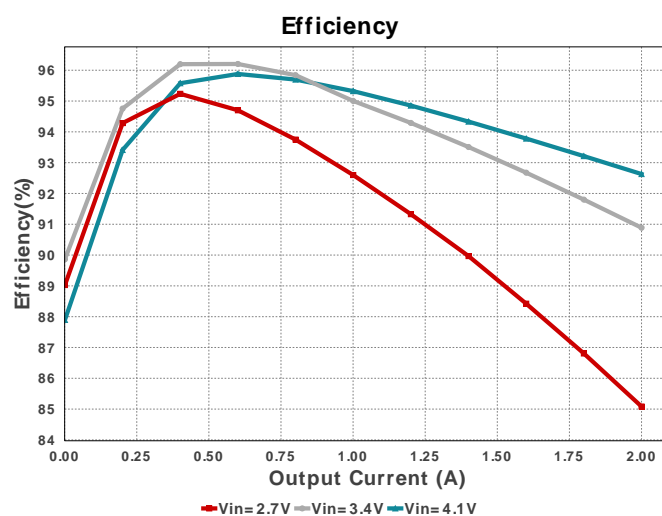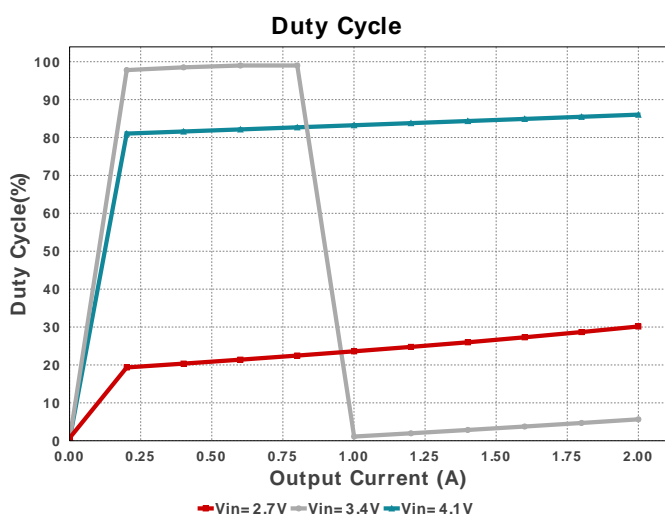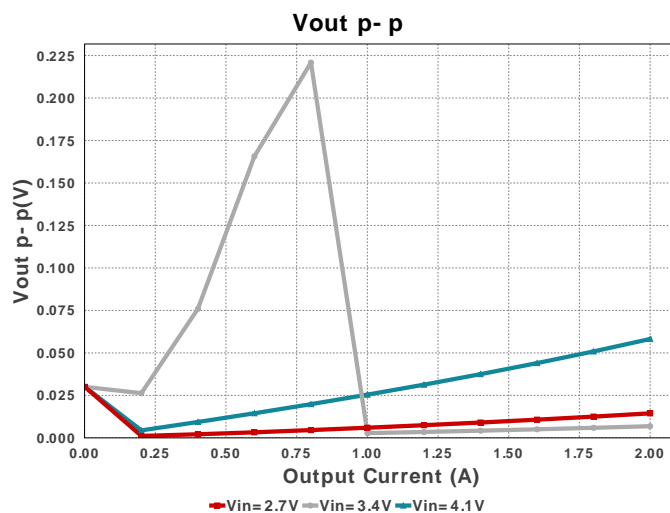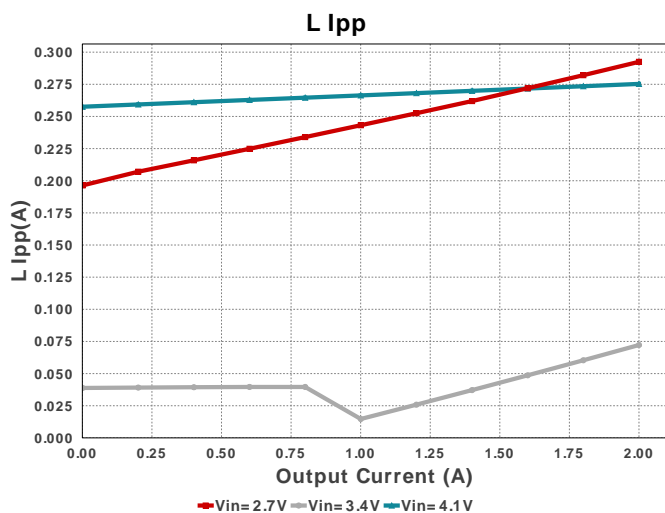

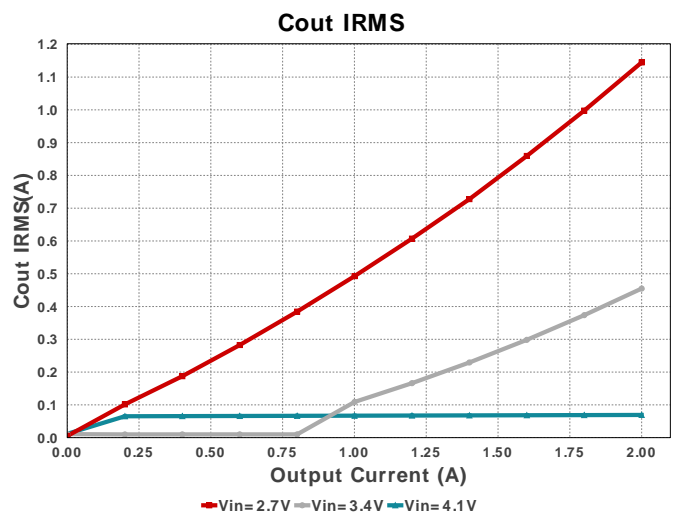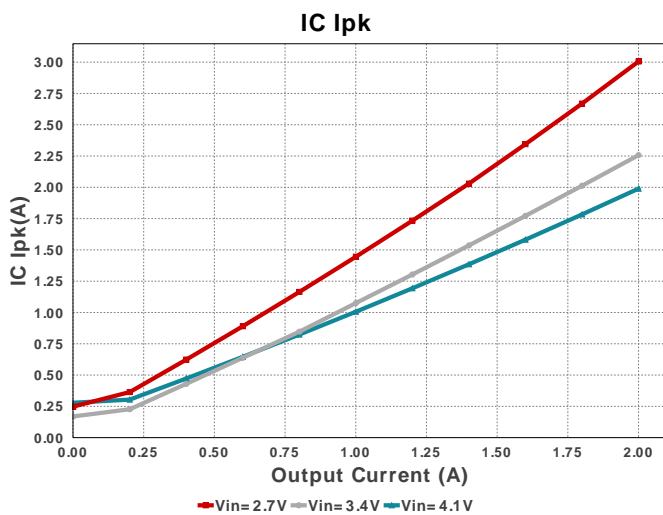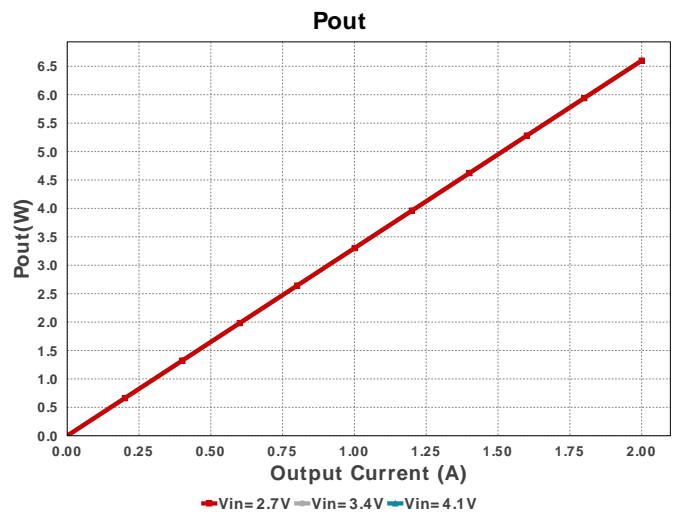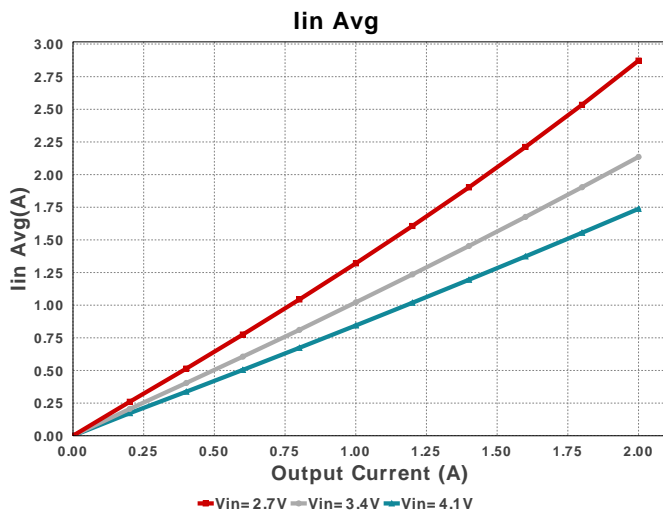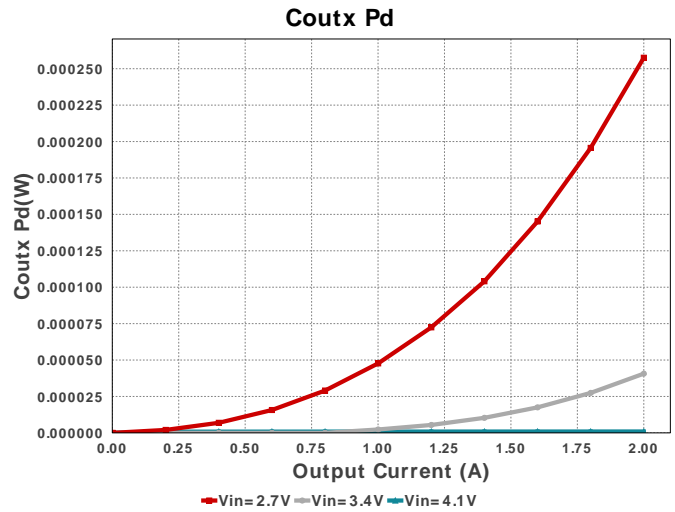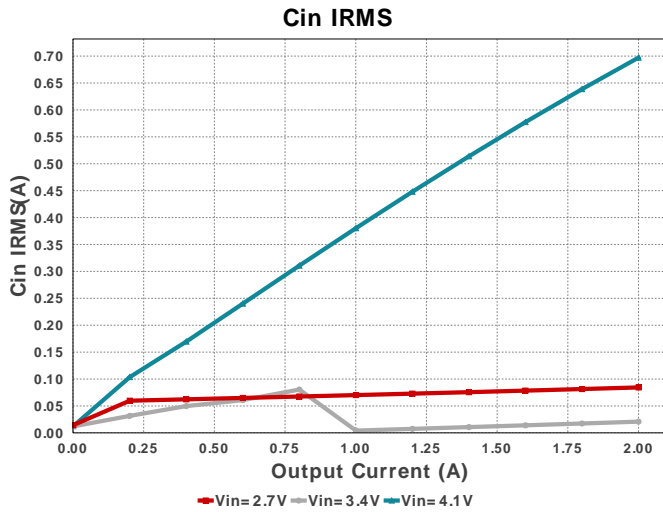

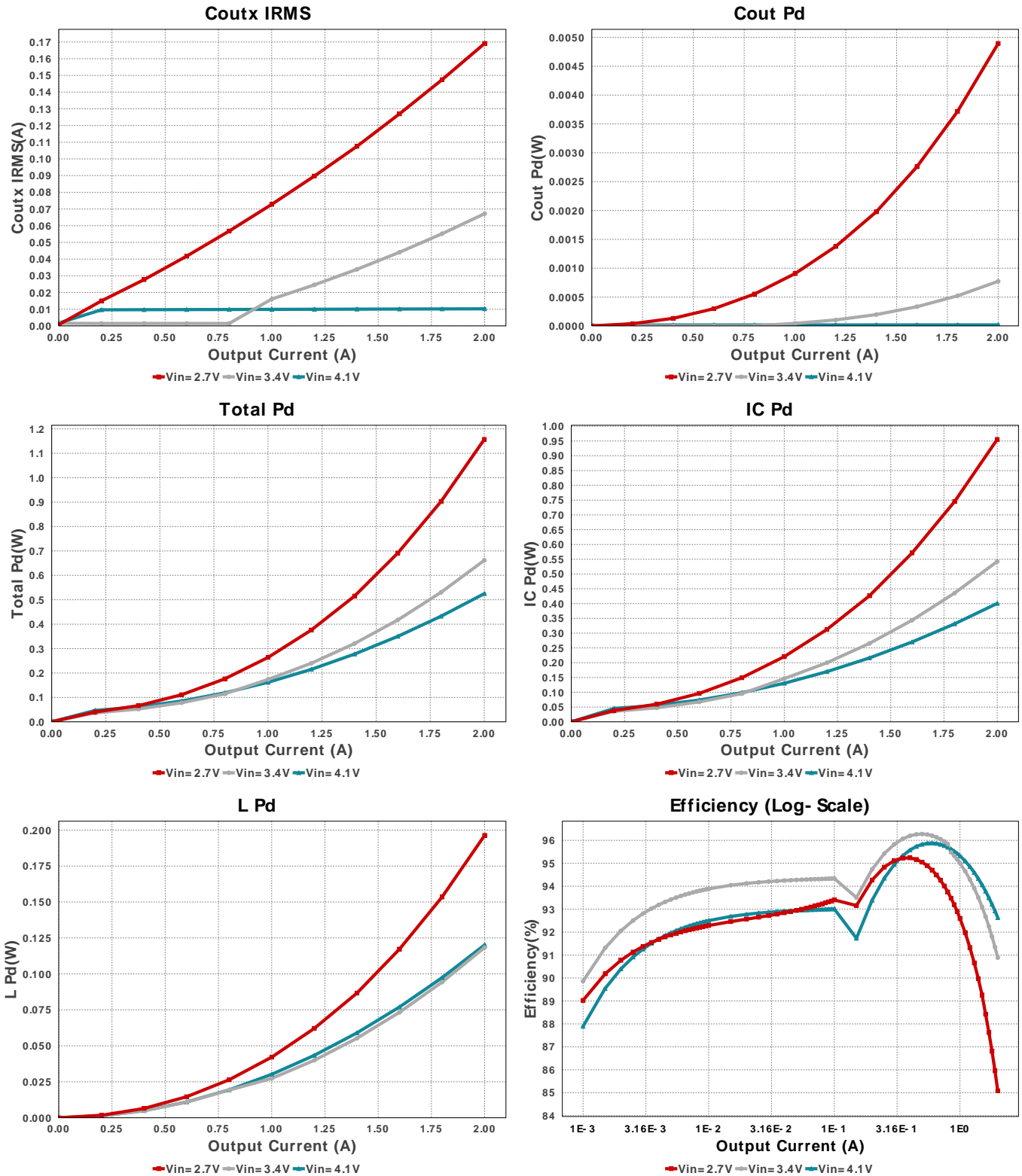

## Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	84.411 mA	Current	Input capacitor RMS ripple current
2.	Cout IRMS	1.144 A	Current	Output capacitor RMS ripple current
3.	Coutx IRMS	169.006 mA	Current	Output capacitor _x RMS ripple current
4.	IC IpK	3.003 A	Current	Peak switch current in IC
5.	Iin Avg	2.87 A	Current	Average input current
6.	L Ipp	292.41 mA	Current	Peak-to-peak inductor ripple current
7.	BOM Count	7	General	Total Design BOM count
8.	FootPrint	57.0 mm <sup>2</sup>	General	Total Foot Print Area of BOM components
9.	Frequency	2.5 MHz	General	Switching frequency
10.	Mode	BOOST PWM CCM	General	PWM/PFM Mode
11.	Pout	6.6 W	General	Total output power

#	Name	Value	Category	Description
12.	Total BOM	\$1.78	General	Total BOM Cost
13.	Vout Actual	3.298 V	Op_Point	Vout Actual calculated based on selected voltage divider resistors
14.	Duty Cycle	30.135 %	Op_point	Duty cycle
15.	Efficiency	85.161 %	Op_point	Steady state efficiency
16.	IC Tj	97.823 degC	Op_point	IC junction temperature
17.	ICThetaJA	71.1 degC/W	Op_point	IC junction-to-ambient thermal resistance
18.	IOUT_OP	2.0 A	Op_point	Iout operating point
19.	VIN_OP	2.7 V	Op_point	Vin operating point
20.	Vout p-p	7.264 mV	Op_point	Peak-to-peak output ripple voltage
21.	Cin Pd	64.127 $\mu$ W	Power	Input capacitor power dissipation
22.	Cout Pd	0.0 W	Power	Output capacitor power dissipation
23.	Coutx Pd	0.0 W	Power	Output capacitor_x power loss
24.	IC Pd	953.904 mW	Power	IC power dissipation
25.	L Pd	196.043 mW	Power	Inductor power dissipation
26.	Total Pd	1.15 W	Power	Total Power Dissipation
27.	Vout Tolerance	1.53 %		Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable

## Design Inputs

#	Name	Value	Description
1.	Iout	2.0	Maximum Output Current
2.	VinMax	4.1	Maximum input voltage
3.	VinMin	2.7	Minimum input voltage
4.	Vout	3.3	Output Voltage
5.	base_pn	TPS630250	Base Product Number
6.	source	DC	Input Source Type
7.	Ta	30.0	Ambient temperature

## Design Assistance

1. **TPS630250** Product Folder : <http://www.ti.com/product/TPS630250> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

**You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.**

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).